
 
 
 


Part I

2. Behaviour

 

3. Invalid input

There is no indeterminate input for the latch and flip-flop, but any starting with the Clk at 0 won't change the state of the circuit at all, and with the 2nd d-latch in the master slave, there won't be any input coming from the previous d-latch.

Part II

a) What would happen if you didn't include the register in your diagram?


The output of the circuit would immediately be routed to the B input, whilst with a register, the register will only let the output through when the clock is high.


a) When multiplying two n-bit binary numbers, how many bits will you need to store the result?

You would need $2n$ bits as an upper bound of the number of bits to store the product of a n-bit multiplication

2. Testing

Function 0

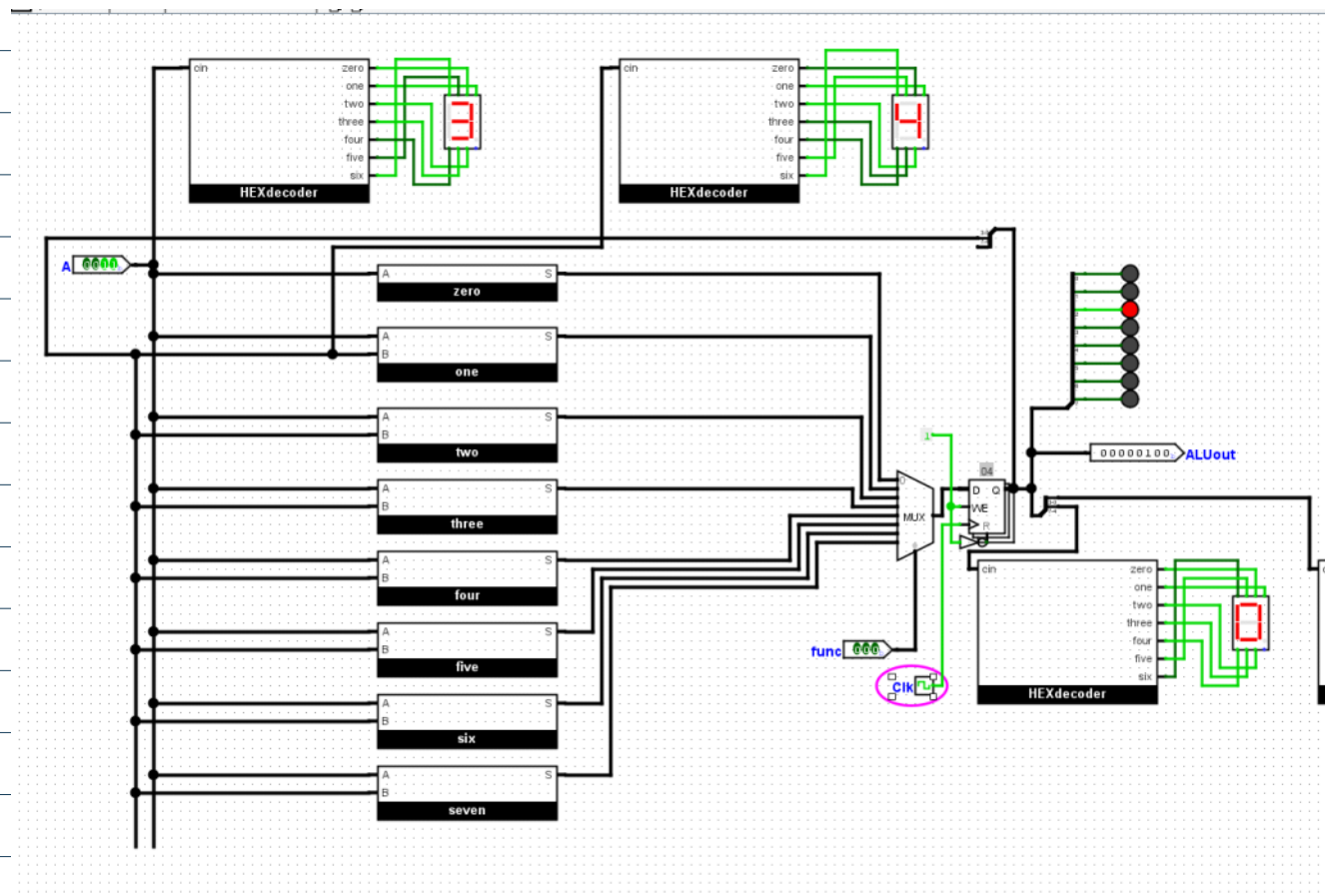


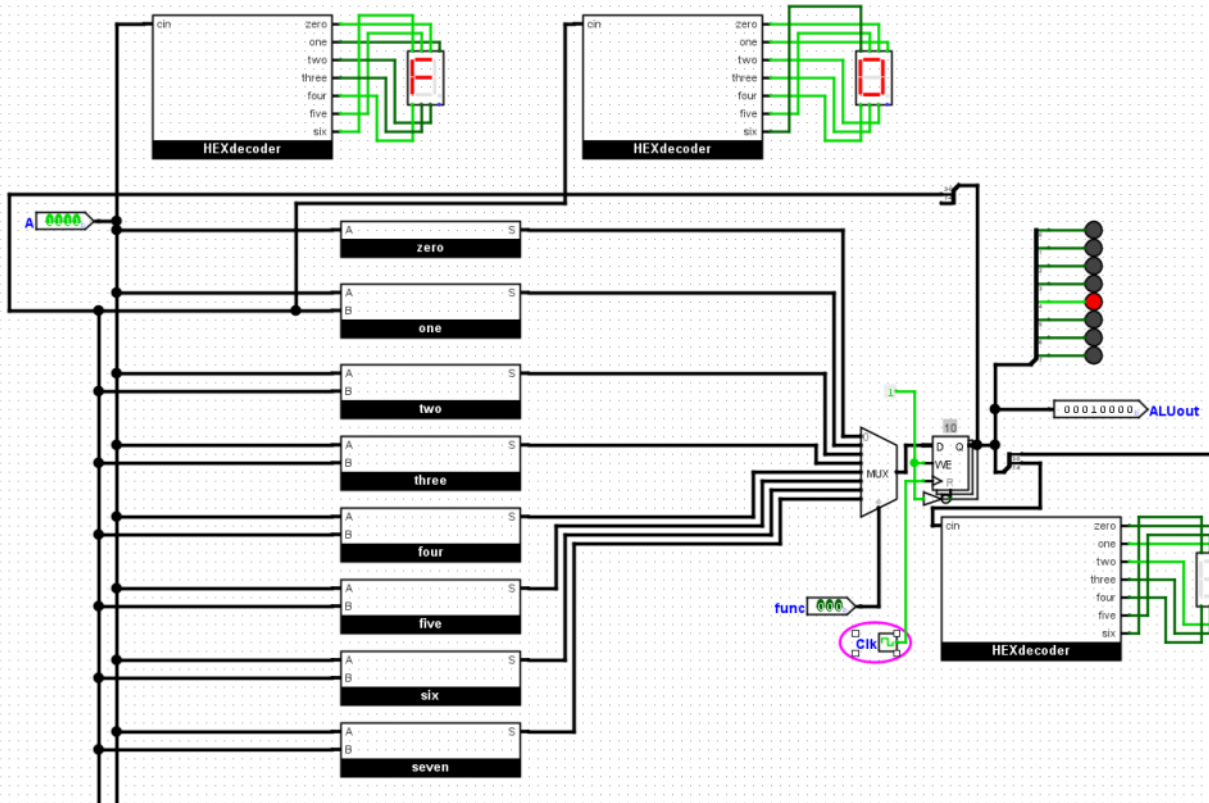

The output to the register is always A + 1 no matter what is stored in the register

Function 1


By constantly changing the state of the clock, the value of the register should keep increasing with the formula of $Ans = A + PrevAns$

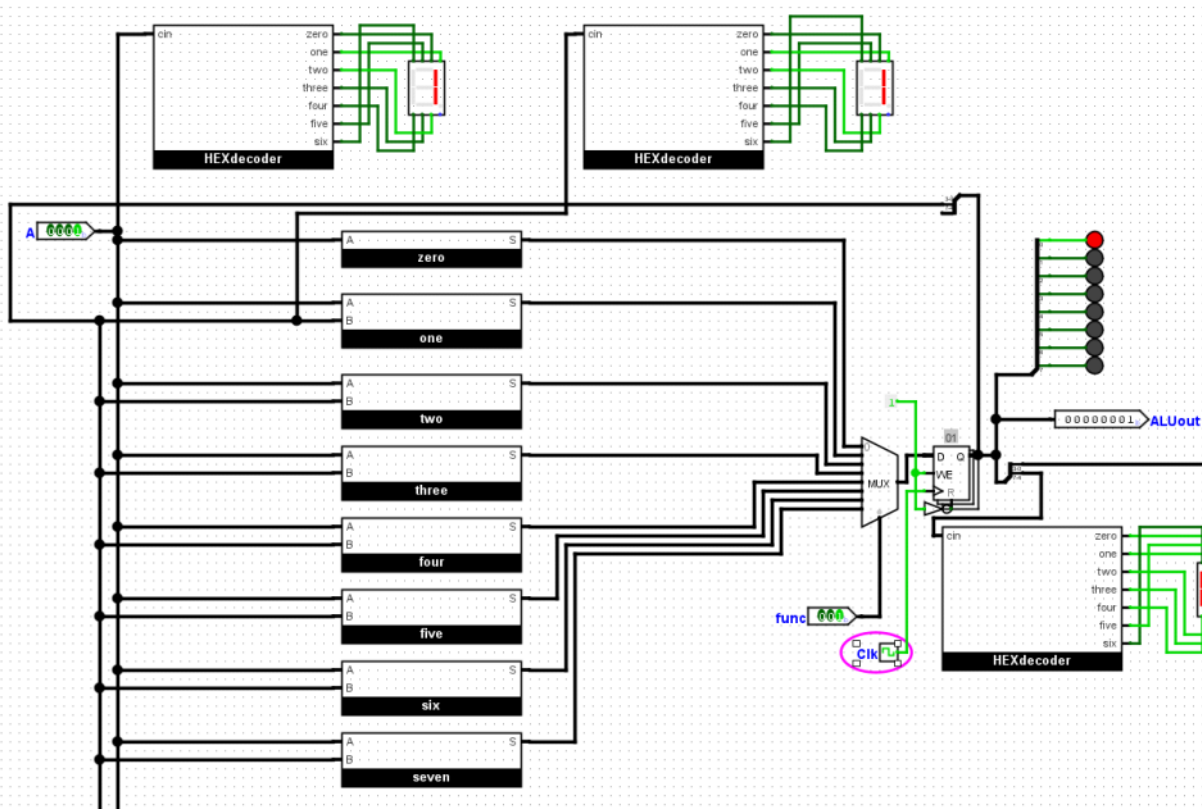


Function 2

Same as function 1

Function 3

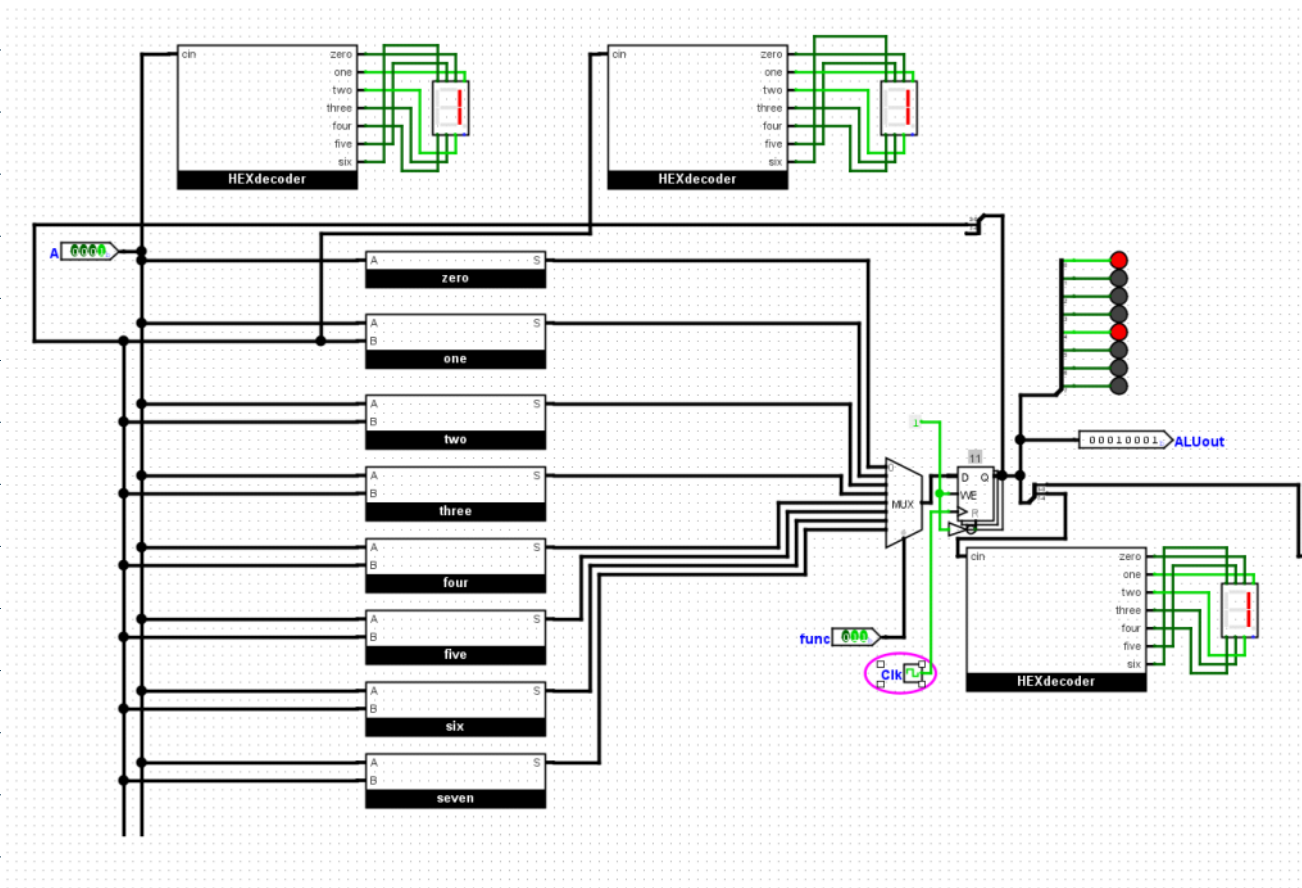

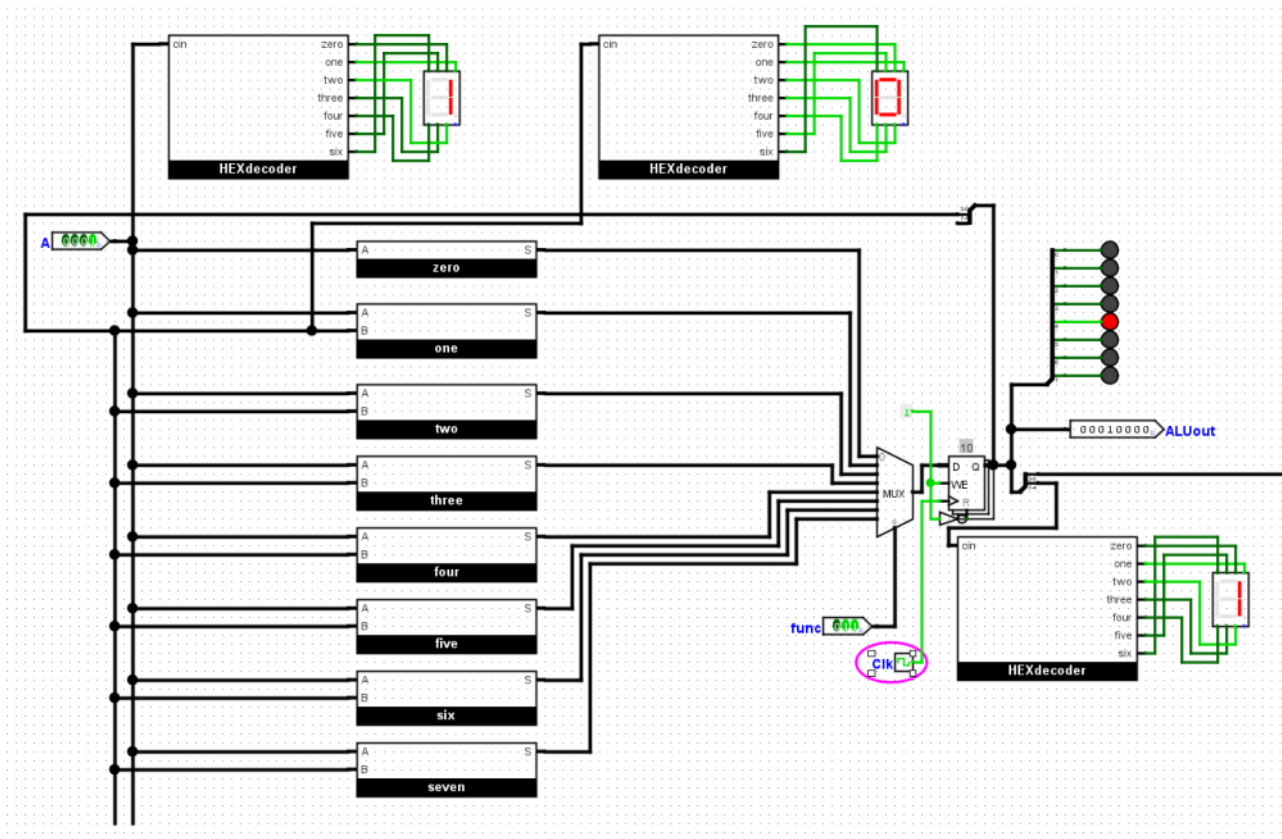


Using A = 0001, the register will store 0001 0000 on the first clock cycle, and repeat between that and 0001 0001 since only the least significant 4 bits are fed back as input B, and the first 4 bits = A XOR B. It will continuously do 0001 XOR 0000 then 0001 XOR 0001, causing the first bit to change on each cycle.

Function 4

As expected, if the register starts with 0, it will always stay 0 if A = 0000
If A is anything but 0, register stores 1 and then since there's a 1 in the input now, the output will stay as 1

Function 5



Set the initial value in the register to 0000 1111, then test the shifting with A = 0001, next clock cycle register should be 0001 1110

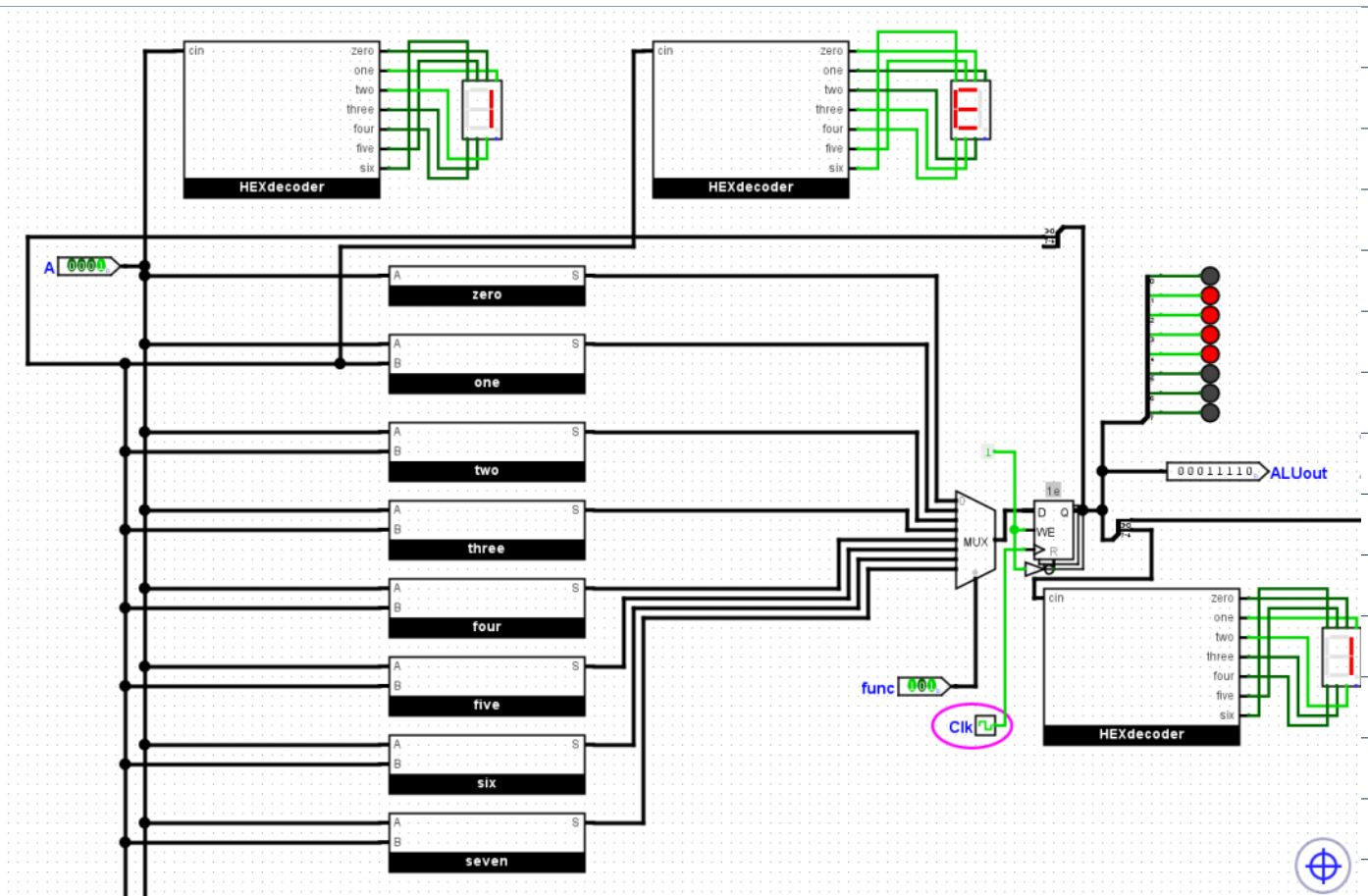

Function 6

Same as function 5, just shifting right instead

Function 7

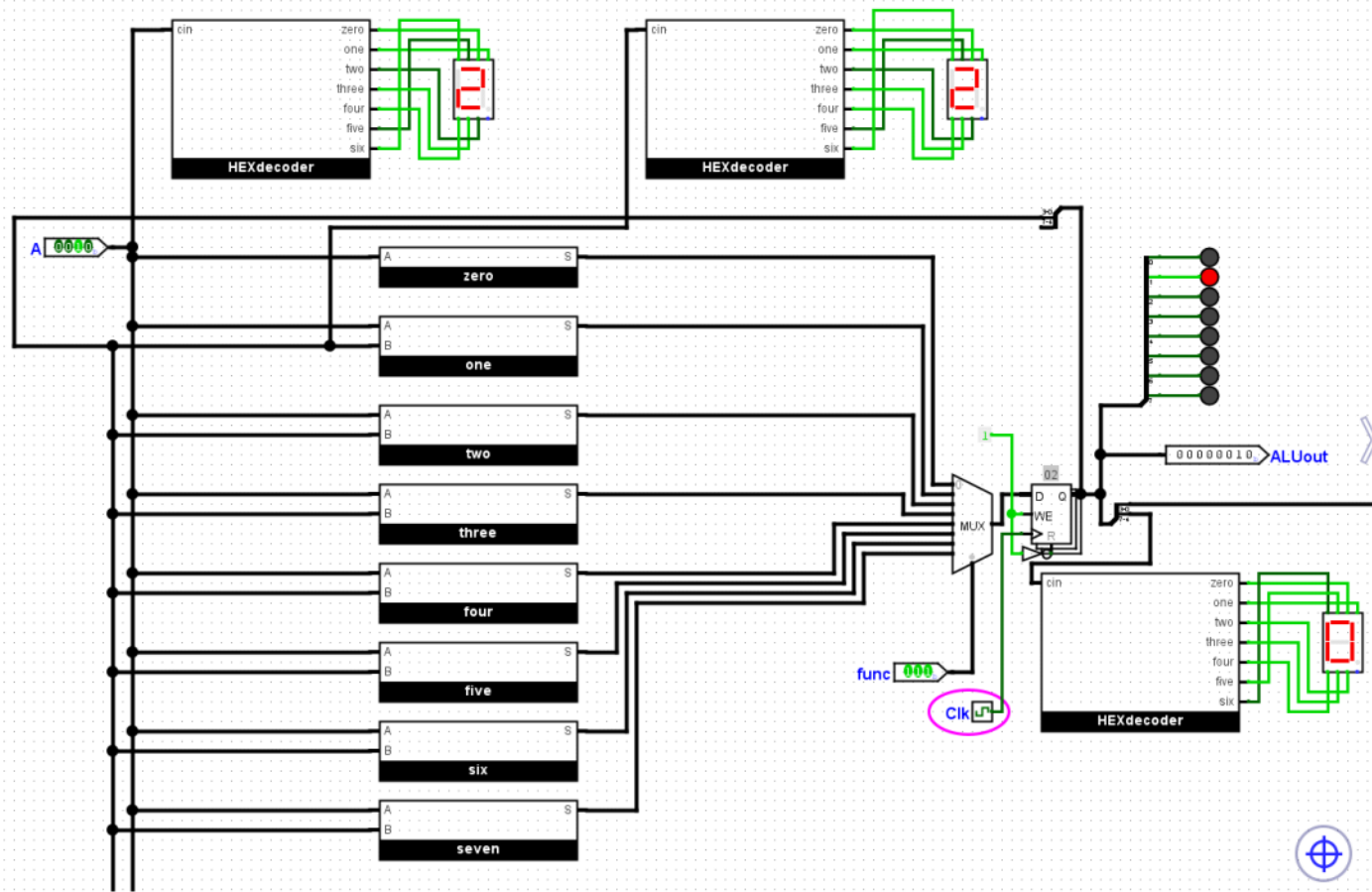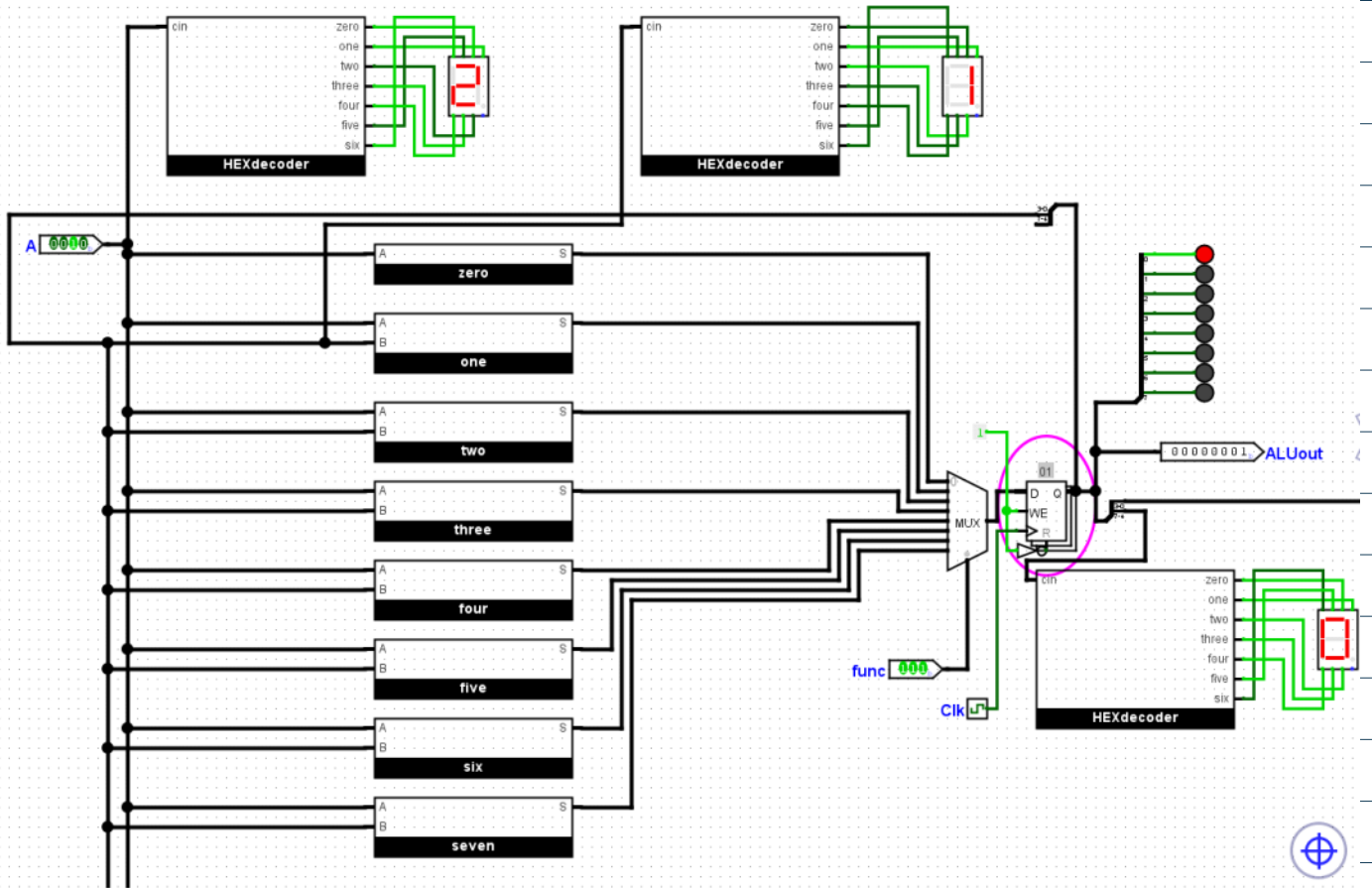

Setting the register to 0000 0001 to start and A = 0010, every clock cycle will shift the 1 down a bit (because of multiplying by 2) up to 0001 0000 because it only routes the first 4 bits back as input B.

Part III

1. Behaviour:

What is the behaviour of the 8-bit shift register shown in Figure 5 when Load n = 1 and ShiftRight = 0 ?


 


Figure 4: Single-bit shift-register


As shown in figure 4, if shift = 0 and load_n = 1, the flip-flop will keep its current output as the same. So on the scale of the 8-bit shift register, all 8 ShifterBits will keep their current value.

2. Schematic

 


5. Simulations


Test 1: Normal loading of load_val

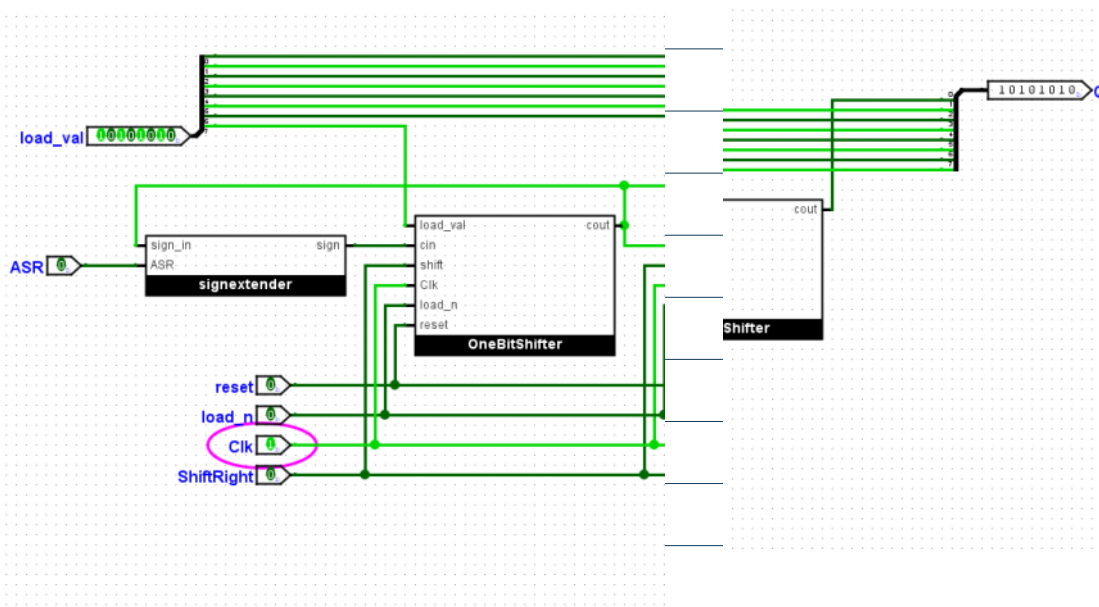


Test 2: Reset all to 0

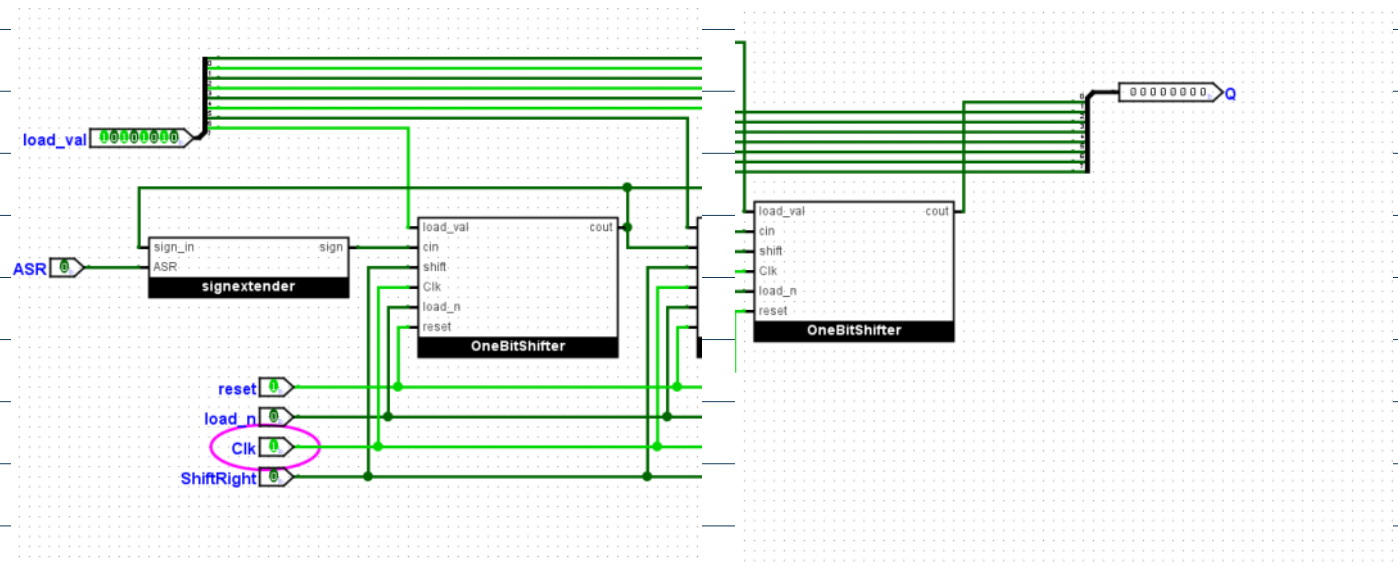


Test 3: Shift right 1 clock cycle

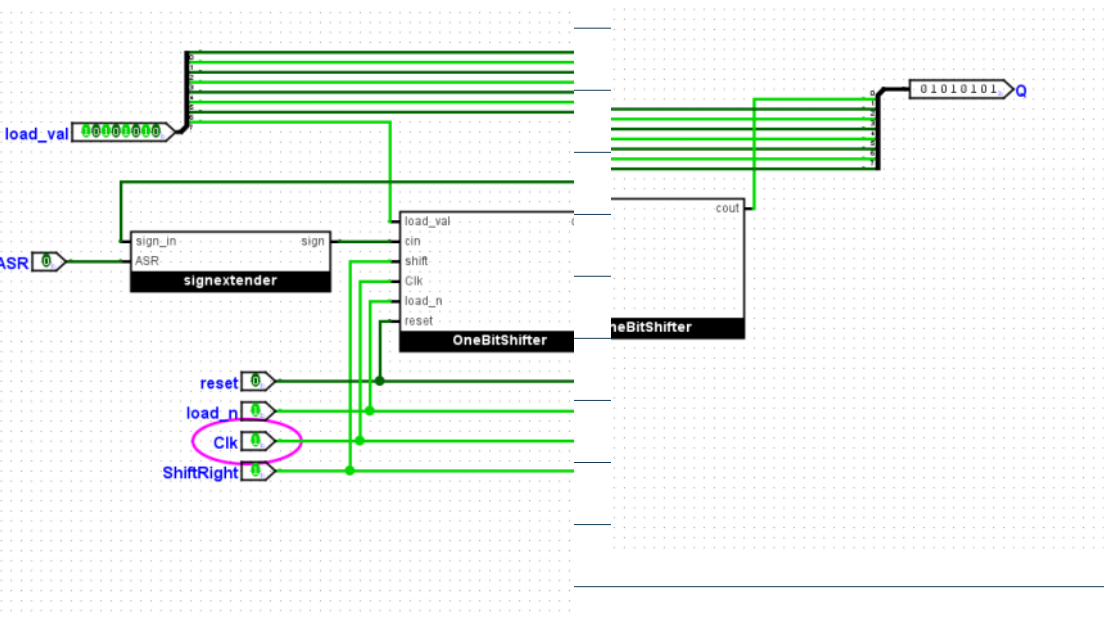

Test 4: Shift right 1 clock cycle with ASR

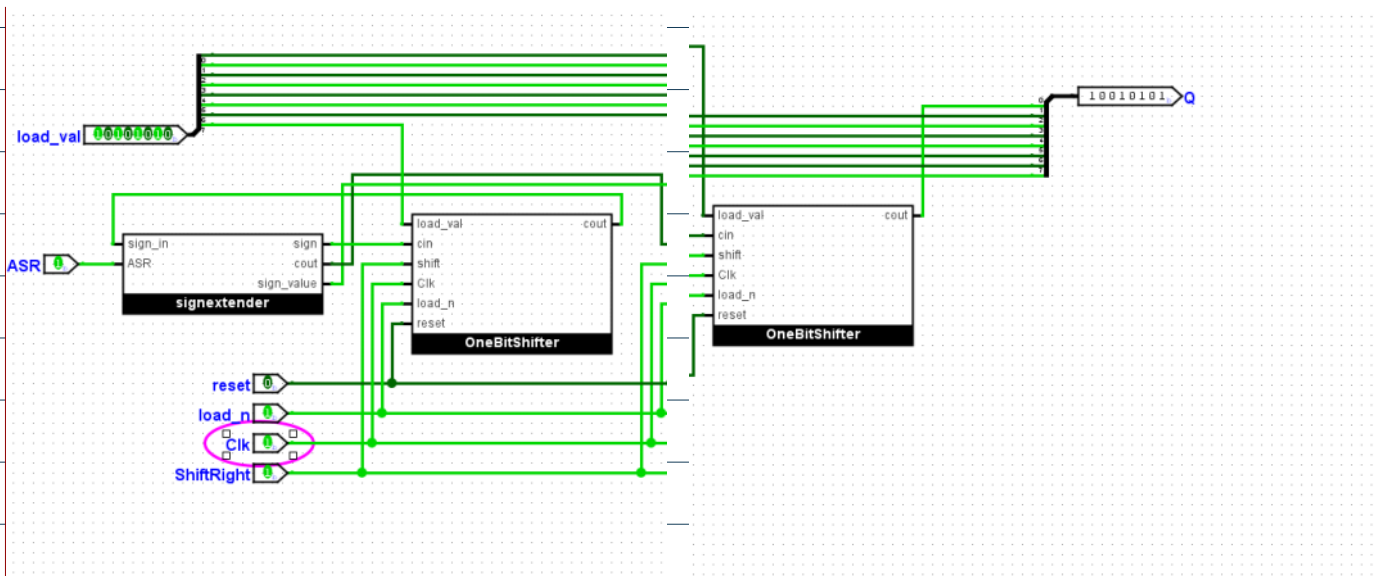

Test 5: ShiftRight without load_n

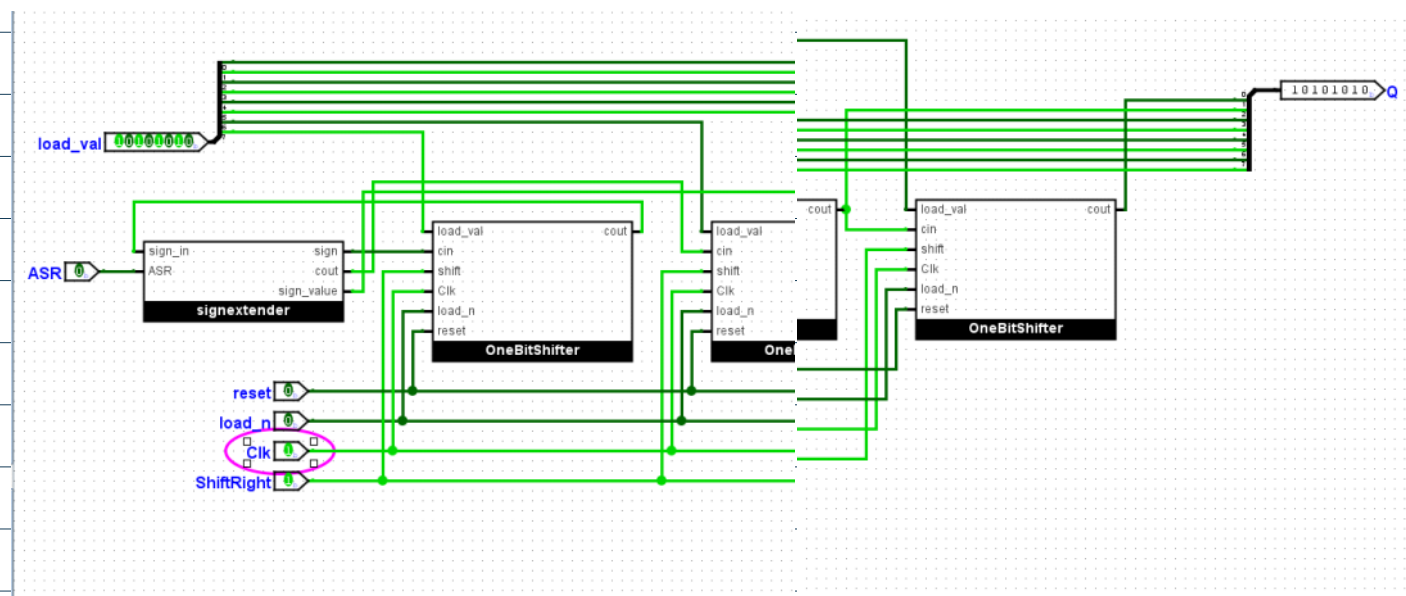

Test 6: Try loading load_vals with load_n = 1

